

# Introduction to Digital Logic

## EECS/CSE 31L

### Assignment 1 Design Report Sample

#### Designing Combinational Circuits

prepared by: Pooria M.Yaghini  
Student ID: 12345678

EECS Department  
Henry Samueli School of Engineering  
University of California, Irvine

October, 18, 2014


## 1 BLOCK Description

This block is designed to get 2 input, perform operation X.

## 2 Input/Output Port Description


Port name	Port size	Port Type	Description
input0	1	IN	gets the first operand
input1	1	IN	gets the second operand
output	1	OUT	will have the operation result

### 3 Design Schematic

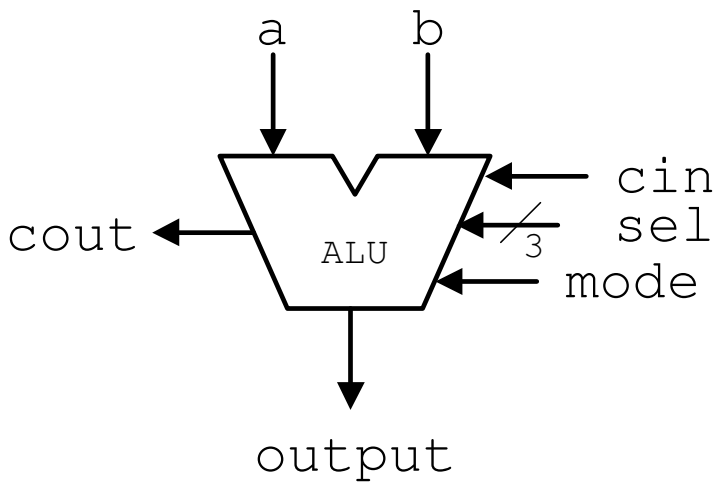

### 4 Expected and Simulation Waveform

Expected Waveform is as follows:

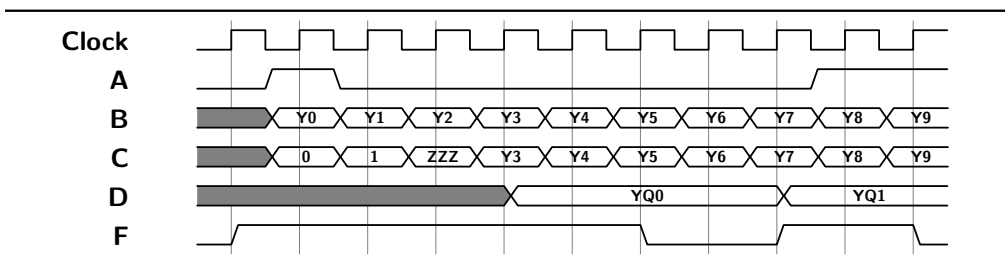

Simulation Waveform is as follows:

