

Introduction to Digital Logic EECS/CSE 31L

Assignment 4 Design Report Designing Register

Prepared by: Derek Yang
Student ID: 63118832

EECS Department
Henry Samueli School of Engineering
University of California, Irvine

November, 8, 2014


1 BLOCK Description

This 32-bit register is designed to receive a 32-bit input and read out the 32-bit input as the 32-bit output if write enable is active. It supports asynchronous and synchronous resets, meaning when the asynchronous signal is enabled, the output will be 0 whether the clock signal is on or off and when the synchronous signal is enabled, the out should be 0 only when the clock signal is on. This design also features an incrementing feature, which increments the output by one.

2 Input/Output Port Description

Port Name	Port Size	Port Type	Description
clk	1	IN	Clock Signal
rst_a	1	IN	Asynchronous Reset Signal
rst_s	1	IN	Synchronous Reset Signal
inc	1	IN	Increment Signal
we	1	IN	Write Enable Signal
din	32	IN	32-bit Input
dout	32	OUT	32-bit Output

3 Design Schematic

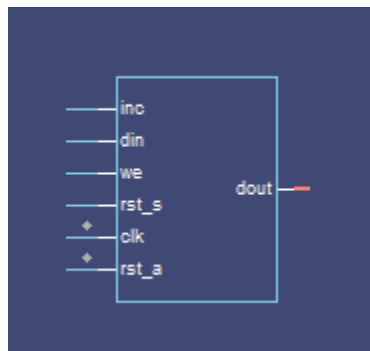

4 Wave Map

