

# Introduction to Digital Logic

## EECS/CSE 31L

### Assignment 1 Design Report Sample

#### Designing Combinational Circuits

prepared by: Derek Yang  
Student ID: 63118832

EECS Department  
Henry Samueli School of Engineering  
University of California, Irvine

November, 11, 2014

## 1 BLOCK Description

This 32-bit ALU is designed to accept two 32-bits and depending on the mode and the opsel selected, it will perform a series of operations to the two 32-bit numbers. The operations include arithmetic operations such as addition, subtraction, increment, decrement, etc. It can also perform logical operations such as AND, OR, XOR, shifts, etc.

## 2 Input/Output Port Description

Port Name	Port Size	Port Type	Description
A	32	IN	1 <sup>st</sup> 32-Bit Number
B	32	IN	2 <sup>nd</sup> 32-Bit Number
opsel	3	IN	Operation Selection
mode	1	IN	Mode Selection (0=Arithmetic, 1=Logical)
output	32	OUT	Output of the operation
cout	1	OUT	Carry out bit

## 3 Design Schematic

