

Derek Yang
63118832

Introduction to Digital Logic
EECS/CSE 31L
Homework 3
Finite State Machine
Course Instructor: Pooria M.Yaghini
Henry Samueli School of Engineering
University of California, Irvine
Nov 22, 2014
Due on Monday 12/01/2014 , 11:30 pm


1 Designing a state machine (points 50)

This question evaluates your ability to write a FSM in VHDL. Based on following entity and Figure1 write the ARCHITECTURE part for this mealy FSM.

```
-----  
library ieee ;  
use IEEE . std_logic_1164 . all ;  
-----  
ENTITY mealy is  
port (  
    clk : IN std_logic ;  
    reset : IN std_logic ;  
    input : IN std_logic ;  
    output : OUT std_logic  
);  
END mealy ;  
-----  
ARCHITECTURE mealy_arch OF mealy IS  
    TYPE state IS (zero, one, two, three);  
    SIGNAL pr_state, nx_state: state;  
BEGIN  
-----Lower Section-----  
    PROCESS(clk, rst)  
    BEGIN  
        IF (reset = '1') THEN  
            pr_state <= zero;  
        ELSIF (clk'EVENT AND clk = '1') THEN  
            pr_state <= nx_state;  
        END IF;  
    END PROCESS;  
-----Upper Section-----  
    PROCESS(pr_state, input)  
    BEGIN  
        CASE pr_state IS  
            WHEN zero =>  
                IF ( input = '0' ) THEN  
                    nx_state <= one;  
                    output <= '0';  
                ELSE  
                    nx_state <= two;  
                    output <= '1';  
                END IF;  
            WHEN one =>  
                IF ( input = '0' ) THEN  
                    nx_state <= three;  
                    output <= '0';  
                ELSE  
                    nx_state <= one;  
                    output <= '0';  
                END IF;  
            WHEN two =>  
                IF ( input = '0' ) THEN  
                    nx_state <= two;  
                    output <= '1';
```

```
ELSE
    nx_state <= three;
    output <= '0';
END IF;
WHEN three =>
    IF ( input = '0' ) THEN
        nx_state <= three;
        output <= '1';
    ELSE
        nx_state <= zero;
        output <= '1';
    END IF;
END CASE;
END PROCESS;
END mealy_arch;
```

Figure 1: FSM model

 

2 Traffic Lights (points 50)

In this question, we complete the traffic light controller example at the end of lecture 6. Please answer the following questions.

I) How many modes of operation are there?

There are 3 modes of operation : regular(clk), test(test) and standby mode(stby).

II) Fill the blanks (A, B, C, D, E and F).

- A. GENERIC
- B. SIGNAL
- C. YY
- D. pr_state, test
- E. r2 <= '1'; y2 <= '0'; g2 <= '0';
- F. END CASE;

III) Which states(RG, RY, GR, YR, YY) belong to each mode of operation?

Regular Mode: RG, RY, GR, and YR.

Test Mode: RG, RY, GR, YR and YY.

Standby Mode: RY, YR and YY.

```
-----
library ieee ;
use IEEE . std_logic_1164 . all ;
-----
```

```
ENTITY tlc IS
  GENERIC(
    timeRG : POSITIVE := 1800;
    timeRY : POSITIVE := 300;
    timeGR : POSITIVE := 2700;
    timeYR : POSITIVE := 300;
    timeTEST : POSITIVE := 60;
    timeMAX : POSITIVE := 2700);
  PORT (
    clk , stby , test , : IN STD_LOGIC ;
    r1 , r2 , y1 , y2 , g1 , g2 : OUT STD_LOGIC );
END tlc ;
-----
```

```
ARCHITECTURE fsm of tlc IS
  TYPE state IS ( RG , RY , GR , YR , YY );
```

Derek Yang

63118832

```
SIGNAL pr_state , nx_state : state ;
SIGNAL timer : INTEGER RANGE 0 TO timeMAX ;
BEGIN
---Lower section of FSM ---
PROCESS ( clk , stby )
VARIABLE count : INTEGER RANGE 0 to timeMAX ;
BEGIN
    IF ( stby = '1' ) THEN
        pr_state <= YY;
        count := 0;
    ELSIF ( clk ' EVENT AND clk = '1' ) THEN
        count := count + 1;
        IF ( count >= timer ) THEN
            pr_state <= nx_state ;
            count := 0;
        END IF;
    END IF;
END PROCESS ;
---Upper section of FSM ---
PROCESS (pr_state, test)
BEGIN
    CASE pr_state IS
        WHEN RG =>
            r1 <= '1' ; y1 <= '0' ; g1 < '0' ;
            r2 <= '0' ; y2 <= '0' ; g2 <= '1' ;
            nx_state <= RY;
            IF ( test = '0' ) THEN
                timer <= timeRG ;
            ELSE
                timer <= timeTEST ;
            END IF;
        WHEN RY =>
            r1 <= '1' ; y1 <= '0' ; g1 < '0' ;
            r2 <= '0' ; y2 <= '1' ; g2 <= '0' ;
            nx_state <= GR;
            IF ( test = '0' ) THEN
                timer <= timeRY ;
            ELSE
                timer <= timeTEST ;
            END IF;
        WHEN GR =>
            r1 <= '0' ; y1 <= '0' ; g1 < '1' ;
            r2 <= '1' ; y2 <= '0' ; g2 <= '0' ;
            nx_state <= TR;
            IF ( test = '0' ) THEN
                timer <= timeGR ;
            ELSE
                timer <= timerTEST ;
            END IF;
        WHEN YR =>
            r1 <= '0' ; y1 <= '1' ; g1 <= '0' ;
            r2 <= '1' ; y2 <= '0' ; g2 <= '0' ;
            nx_state <= RG;
            IF ( test = '0' ) THEN
                timer <= timeYR ;
            ELSE
                timer <= timeTEST ;
            END IF;
        WHEN YY =>
            r1 <= '0' ; y1 <= '1' ; g1 < '0' ;
            r2 <= '0' ; y2 <= '1' ; g2 <= '0' ;
            timer <= timeTEST ;
            nx_state <= RY;
    END CASE;
END PROCESS ;
END fem ;
-----
```