

Introduction to Digital Logic EECS/CSE 31L

Assignment 4 Design Report Designing Counter

prepared by: Derek Yang
Student ID: 63118832

EECS Department
Henry Samueli School of Engineering
University of California, Irvine

November, 8, 2014


1 BLOCK Description

This 32bit counter takes a 32bit input and counts up or down depending on the ascending mode given, 0 meaning decrement and 1 meaning increment. This counter circuit is also synchronous, meaning it will rely on the clock cycle to take action, so only when the clock is 1, the counter will increment or decrement. The preload mode also enables the user to load their input into the counter. There is also a reset mode, where when enabled, all inputs and counts will return to 0.

2 Input/Output Port Description

Port Name	Port Size	Port Type	Description
clk	1	IN	The Clock Cycle
rst_s	1	IN	Synchronous Reset Signal (1 = Reset)
asc	1	IN	Ascending Signal (0 = Decrement, 1 = Increment)
preload	1	IN	Mode Selection (0=Arithmetic, 1=Logical)
din	32	IN	32-bit Input
dout	32	OUT	32-bit Output

3 Design Schematic

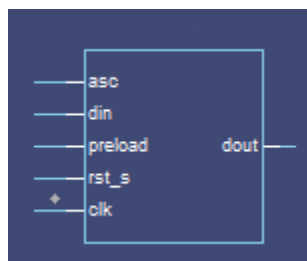

4 Wave

