# Introduction to Digital Logic EECS/CSE 31L

## Assignment 4 Design Report Designing RAM

Prepared by: Derek Yang Student ID: 63118832

EECS Department
Henry Samueli School of Engineering
University of California, Irvine

November, 15, 2014


#### 1 BLOCK Description

This is a 32-bit RAM that can read and write a 32-bit number in 2048 different addresses. It has a chip select option which allows the user to select which chip the RAM will be using as well as a output disable to stop the RAM from reading a number. The read and write function cannot run at the same time, so this RAM can either read or write at a given time.

#### 2 Input/Output Port Description

Port Name	Port Size	Port Type	Description				
addr	11	IN	Address location				
rw	1	IN	Read/Write Enable				
csb	1	IN	Chip Selector				
oeb	1	IN	Output Disabler				
dataIO	32	IN/OUT	Signal for Input and Output				

### 3 Design Schematic

 

#### 4 Wave

11'h001		11'h003				11'h001		11'h000			
(32'h00000	2'h00000001 (3		003	32'h000000	003	32'h00000001		32'h000000000		32'h00000001	